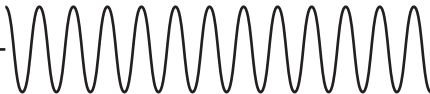


L



R



I_0

A vertical arrow pointing upwards, indicating the direction of current flow in the circuit.